



DEPARTMENT OF INFORMATION SYSTEMS AND COMPUTER SCIENCE

More Combinational Logic

Programmable Logic




```
00101110101000111010111100100111010101101001000101
1101010111010101000010101010100101010101010101010
1010010100100100101010101010101010101010101010101010
1110000111101011000000011110101010101010000010101
11101010111100101000100101111010100010100100111010
1010100101001001001000010101011010101010101010010111
00101010010101001010100000001010101001111101000011001
1000110010000111100110101011000100110101010000101010
1100101010101000010011001010100010010101010101010
1010010100100100101010101010101010101010101010101010
1110000111101011000000011110101010101010000010101
0010010101001010010010100100010101010101001010010
1001010010000101010010010101001010010101010010010
1001010010101001010010101001010010101001001001001
1001010101010010101010101001010010101001001001001
10010101010100101010101010010101010100101010101010
```

									01
									02
									03
									04
									05
A	B	C	D	E	F	G	H		

Lecture Time!

- Logic: Same Rules Apply
- Muxes and Demuxes: Controlling Output
- ROMs and PLAs: Programmable Logic

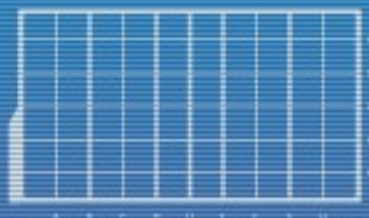00101010010101000011110100001100
10001100100001111001101010010101
11001010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010101010101010101



Combinational Logic Tricks

- Remember, rules in Boolean algebra apply to digital hardware as well!
- XOR can be used for encryption/decryption!
 - But easily broken since the key can be obtained if you have both the actual and encrypted text.

- Plaintext:

011101010101011101000100101000001011100

- Key:

111010100101110001010100000010101111010

- Ciphertext:

10011111000010110001000010110100100110

00101010010101000011110100001100
10001100100001111001101010010101
110010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010100101010010101




DISCS


Multiplexer (Mux, Selector)

- Select 1 out of many inputs.
 - “Many to 1”
- $F = A_s$
 - Implementation of the 2-way mux?
 - Generate truth table first?
 - What about for the 4-way?

2-way mux

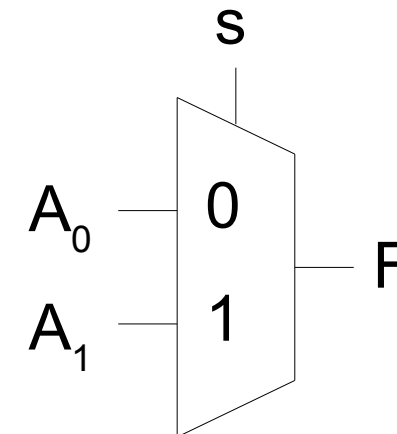

4-way mux

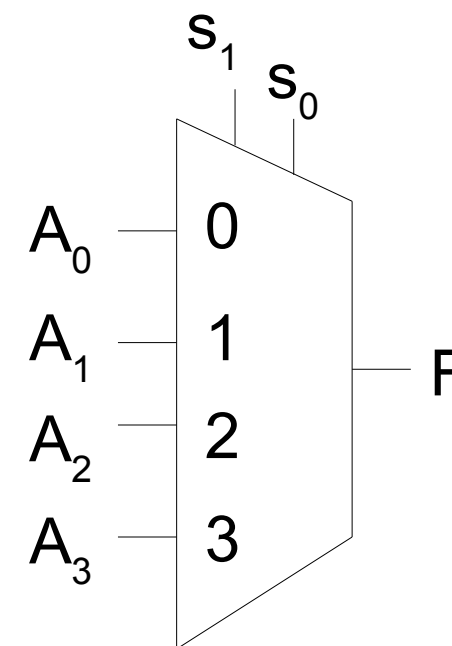


00101010010101000011110100001100
10001100100001111001101010010101
11001010101010100001001100101010100
100101001001001010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
1001010010101001010101010010101




DISCS

Multi-bit Wires / Busses

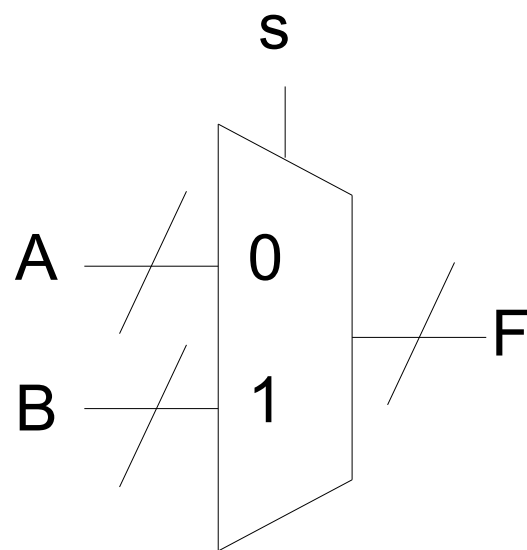- If you need to choose from one of two different X-bit inputs, it might take a while to draw X 2-way multiplexers...
 - You should use the multi-bit notation indicated below.
 - Actual implementation of the multi-bit multiplexer below is still X 2-way muxes, though.



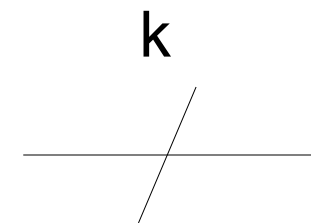k-bit wire
(writing k is
sometimes optional)



00101010010101000011110100001100
10001100100001111001101010010101
110010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
1001010010101001010101010010101



Demultiplexer (Demux)

- Pass input to one of many outputs.


– “1 to Many”

- $F_s = A$, $F_i = 0$ where $i \neq s$


– Implementation of the 2-way demux?

- Generate truth table first?
- What about for the 4-way?

2-way demux

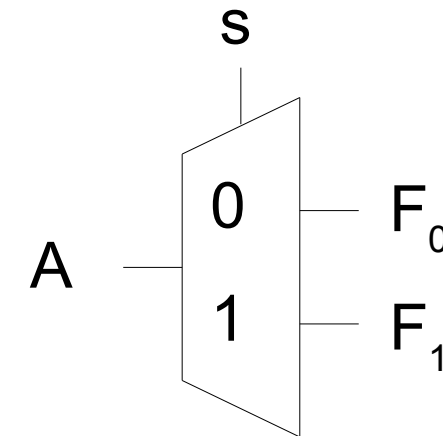

4-way demux

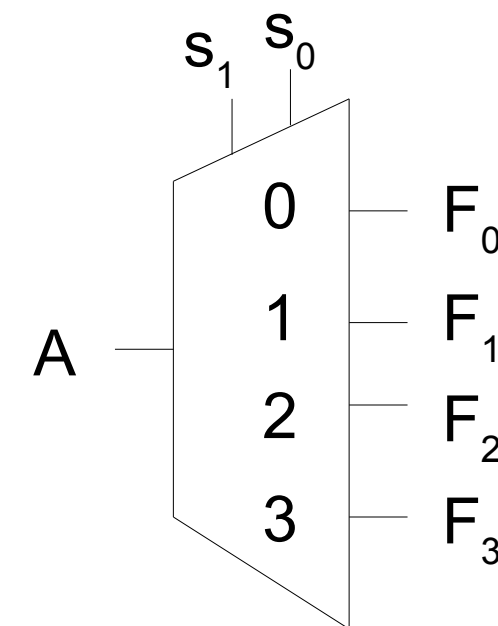

00101010010101000011110100001100
10001100100001111001101010010101
11001010101010100001001100101010100
100101001001001010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010101010101010101




DISCS


Decoder

- Assert exactly one of many outputs.
- $F_s = 1, F_i = 0$ where $i \neq s$
 - Implementation is similar to a demux, but input A is tied to 1.
 - Technically has no multi-bit version.

2-way decoder

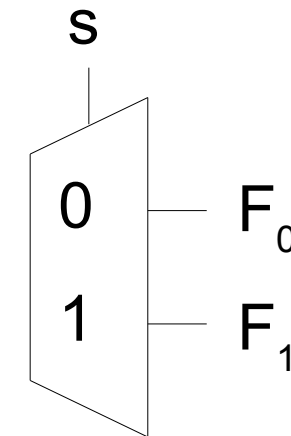

4-way decoder

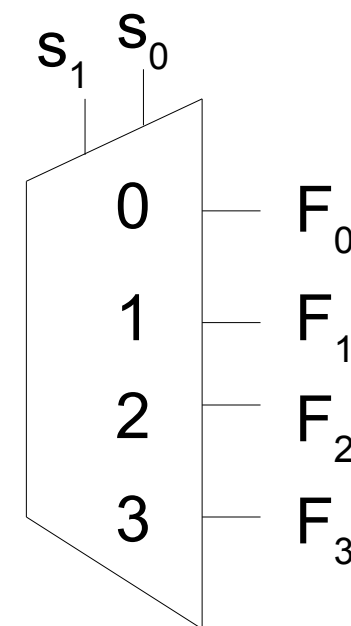


00101010010101000011110100001100
10001100100001111001101010010101
11001010101010100001001100101010100
100101001001001010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010101010101010101



DISCS

Read-Only Memory (ROM)

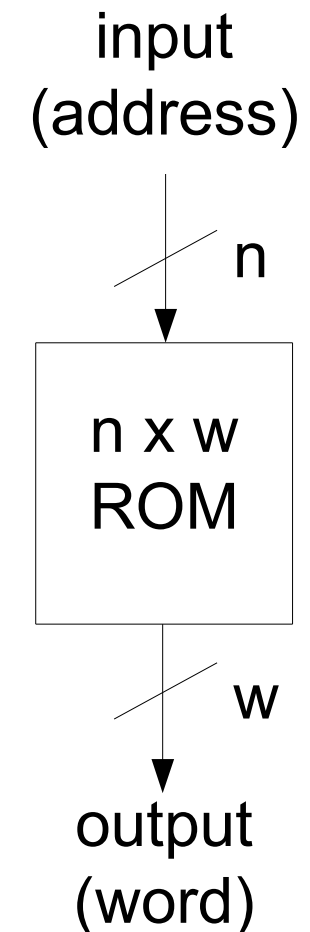- Sometimes, we need PROGRAMMABLE logic.
 - Simplest form: ROM
- ROM is like a big table:
 - Input is composed of n bits, called an “address”.
 - Outputs is composed of w bits, called a “word”.
 - w is called bit-width or wordsize.
 - Can be used to remember words of data or to do functions.





00101010010101000011110100001100
10001100100001111001101010010101
110010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
1001010010101001010101001010101



ROM Implementation

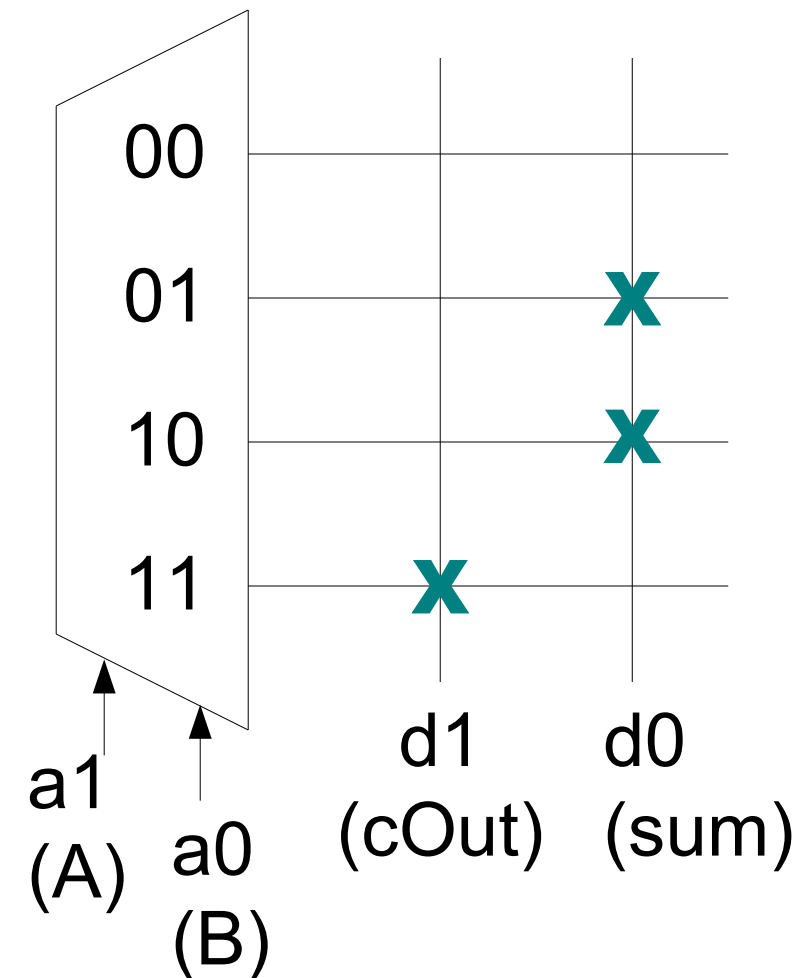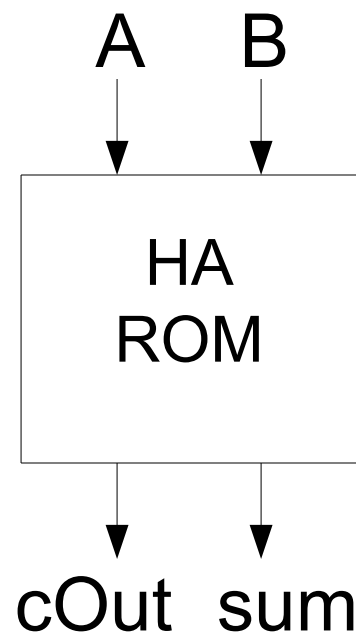- ROM is just a two-dimensional array of 0's and 1's.
- Example: Half adder




00101010010101000011110100001100
10001100100001111001101010010101
11001010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
1001010010101001010101010010101



ROM Logic

- ROM is just a truth table in hardware!
- Any n -input function can be built using ROM w/ n -bit address (since you can choose whatever output you want given specific inputs).
- ROM with w -bit wordsize computes w funcs at the same time.
- No need to minimize, since doing so won't affect actual implementation anyway.

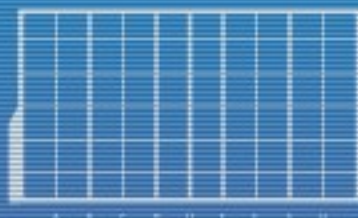
00101010010101000011110100001100
10001100100001111001101010010101
11001010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010101010101010101



Programming ROMs

- ROM is programmed by “burning-in” connections.
 - ROM: burned-in by manufacturer (rare today, but remember cartridge-based consoles?).
 - PROM: can burn each bit only once (programmable).
 - EPROM: can “unburn” by exposing to UV light (erasable).
 - EEPROM: one type is the flash memory, found in USB flash drives (electrically erasable).
- Total size/cost is proportional to total # of bits on right side of truth table (rows*columns).
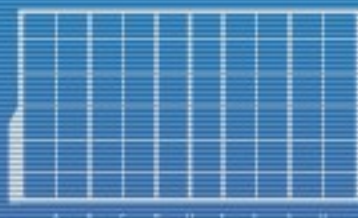
```
00101010010101000011110100001100
10001100100001111001101010010101
110010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
00100101010010100100100100100110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010101010101010101
```



Some ROM Questions


- How many different ways can you program a 2 x 3 ROM?
 - How about a $n \times w$ ROM?
- Design a ROM for a full-adder:
 - What size ROM do you need?
 - What's n ?
 - What's w ?
 - What's the truth table?
 - Draw ROM circuit?
- What size ROM do you need for a 4-bit adder/subtractor?

00101010010101000011110100001100
10001100100001111001101010010101
110010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
1001010010101001010101001010101



Programmable Logic Array (PLA)

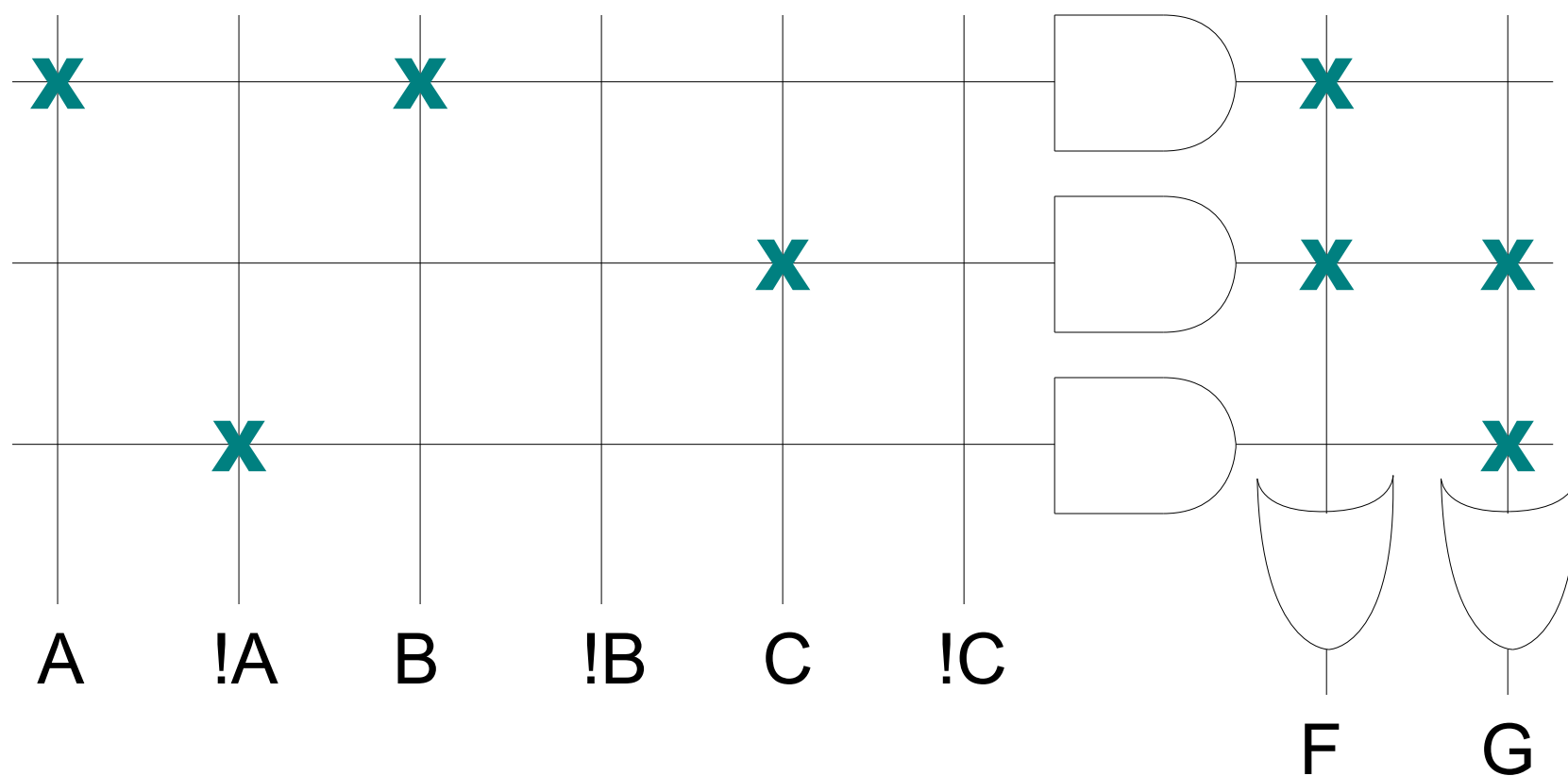- PLA exploits structure of expression.
 - In PLA, # of rows == number of distinct Product Terms.
 - In ROM, # of rows == all 2^k possibilities for k inputs.
- PLAs use less space for more functions than ROMs!



00101010010101000011110100001100
10001100100001111001101010010101
110010101010100001001100101010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010100101010010100101010010101



DISCS