



# DEPARTMENT OF INFORMATION SYSTEMS AND COMPUTER SCIENCE



```
0010111010100011101011110010011101010101001000101
1101010110101010000101010101001010101010101010
10100101001001001010101010101010101010101010101010
1110000111101011000000011110101010101010000010101
11101010111100101000100101111010100010100100111010
1010100101001001001000010101011010101010101010010111
0010101001010100101010000001010101001111101000011001
1000110010000111100110101011000100110101010000101010
1100101010101000010011001010100010010101010101010
10100101001001001010101010101010101010101010101010
1110000111101011000000011110101010101010000010101
0010010101001010010010100100010101010101001010010
10010100100001010100100101010010100101010010010010
1001010010101001010010101001010010101001001001001
100101010101001010101010100101010101010010101010
```

										01
										02
										03
										04
										05
A	B	C	D	E	F	G	H			


# Feedback, State, and Memory

Cyclic Circuits – Can They Work?

# Adding a column of N numbers


- ▶ Form tree of adders?
- ▶ Delay is  $O(\log_2 N)$
- ▶ Size grows as  $O(N)$ 
  - ▶  $(N/2) + (N/4) + (N/8) \dots = N-1$
  - ▶ or,  $1 + 2 + 4 + 8 + 16 + \dots + N/2 = N-1$
  - ▶ or, think of it as a tennis tournament: each player loses *exactly* once except for champion. Therefore,  $N-1$  matches.

## Combinational

 

- ▶ **Not scalable to arbitrary N!**
  - ▶ **Need infinite hardware!**
- ▶ **Not practical for general CPU.**

 00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
0010010101001010010010010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS


# Adding a column of N numbers

- ▶ Use an “accumulator”?
  - ▶ *Remember* previous value and feed it to next input: NEED MEMORY
- ▶ Called “Sequential”
  - ▶ Because things happen “in sequence” over time.
- ▶ Size is constant!
- ▶ Delay is  $O(N)$  “cycles”
- ▶ A bit slower, but definitely more practical and scalable to arbitrary N.

## Sequential

 

 001010100101010000111110100001100  
10001100100001111001101010010101  
110010101010100001001100101010100  
1001010010010010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS



 
# Implementing Memory: Inverter Ring?

- ▶ Odd-number cycle --- unstable: values always change



$$V_y = \overline{\text{old } V_x} = \text{new } V_x \quad \leftarrow \text{oscillates!}$$

 - ▶ Even-number cycle --- stable (?): values don't change




$$V_y = \text{INVERT}(\text{INVERT}(V_x))$$

$$V_y = V_x$$

(potentially) stable


 
00101010010101000011110100001100  
10001100100001111001101010010101  
110010101010101000010011001010100  
1001010010010010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
100101010101010010101010010101




DISCS
  
# A Closer Look

- ▶ 3 points on output curve where  $V_Y = V_X$
- ▶ Stable 0 and 1 (2 points)
  - ▶ Slight deviation away from stable point will get pushed back by high-gain part.
  - ▶ Value will hold. (Slight deviations will correct themselves.)
- ▶ Metastable state (3<sup>rd</sup> point)
  - ▶ Slight deviation will push it quickly to either 0 or 1.



 0010101001010100011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS

 
# Metastability

- ▶ Like having a ball balanced on a hill:


- ▶ Probability of staying metastable gets exponentially small in time, but always non-zero.
- ▶ There is always a tiny chance that it will remain metastable no matter how much time passes.



 - ▶ Caused by feeding forbidden values into loop.
  - ▶ Therefore, avoid doing so.



 00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS

# Setting 0 or 1: the SR Latch


- ▶ Problem with Inverter Ring: No inputs!
- ▶ Even if it works:
  - ▶ Need “controllable” inverters!

## ▶ NOR



- ▶ 1 -> always 0

 

- ▶ 0 -> inverter

 


- ▶ Control configuration via S and R.

  

$S$	$R$	$Q$
$0$	$0$	$Q_{old}$
$0$	$1$	$0$
$1$	$0$	$1$
$1$	$1$	$0$

 00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



DISCS




# NOR-NOR SR Latch

►  $S=0, R=0 \rightarrow$  “Latch”


► Inverter loop

►  $Q = Q_{old}$  (keep old value)

 

$S$	$R$	$Q$
0	0	$Q_{old}$
0	1	0
1	0	1
1	1	0

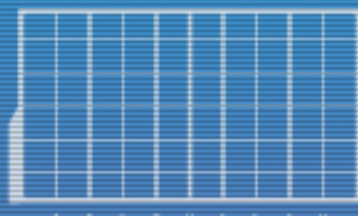00101010010101000011110100001100  
10001100100001111001101010010101  
110010101010100001001100101010100  
1001010010010010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



DISCS




# NOR-NOR SR Latch

►  $S=0, R=1 \rightarrow$  “Reset”


► N2 output always 0

►  $Q = 0$

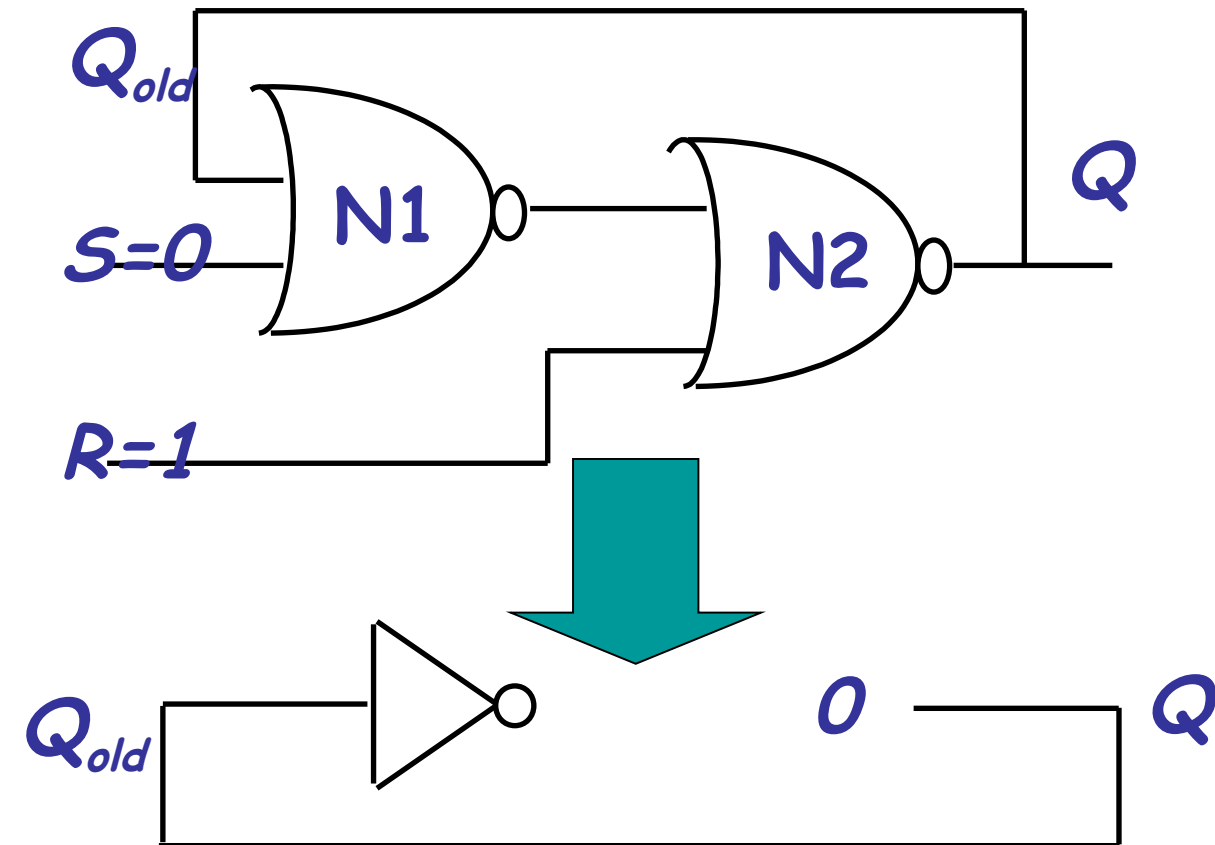

$S$	$R$	$Q$
0	0	$Q_{old}$
0	1	0
1	0	1
1	1	0

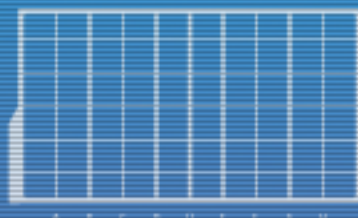00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS
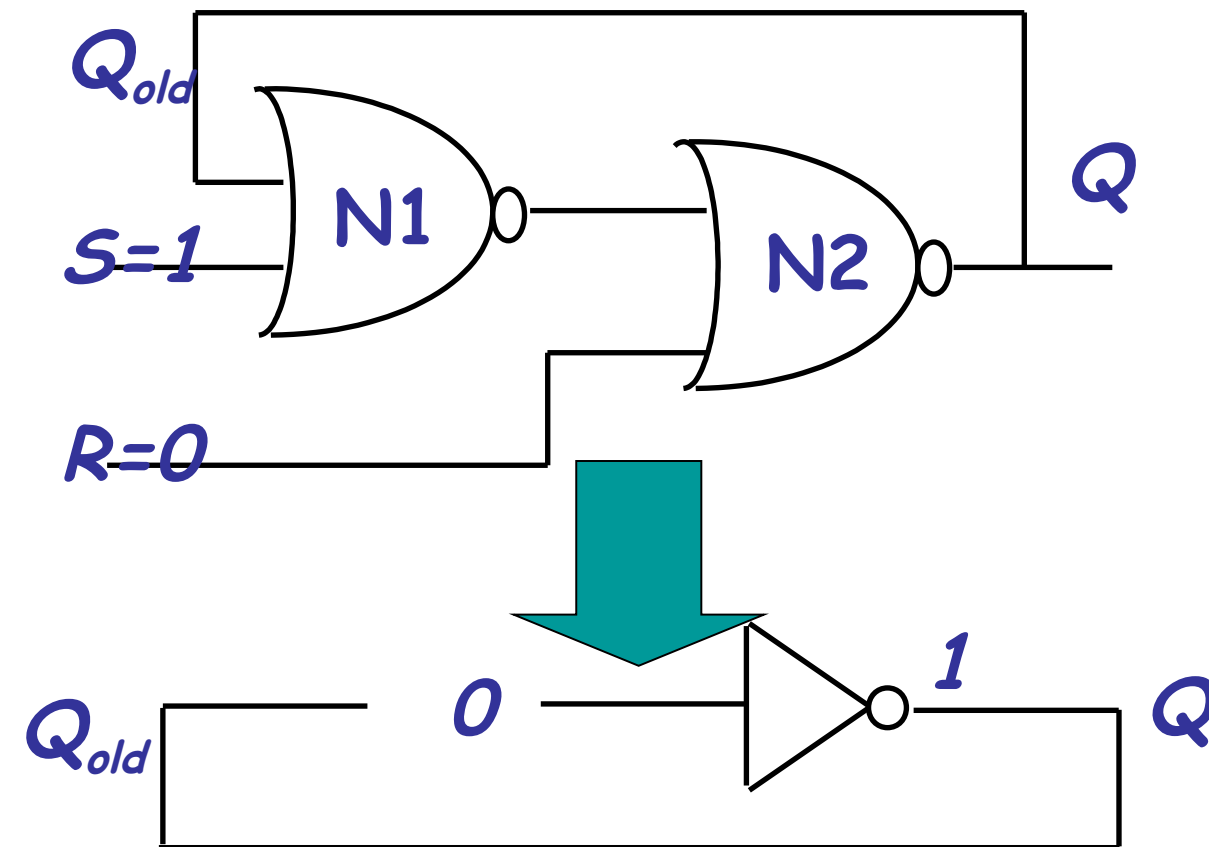
# NOR-NOR SR Latch


►  $S=1, R=0 \rightarrow$  “Set”

► N1 output always 0, N2 inverts  $\rightarrow Q = 1$



$S$	$R$	$Q$
0	0	$Q_{old}$
0	1	0
1	0	1
1	1	0

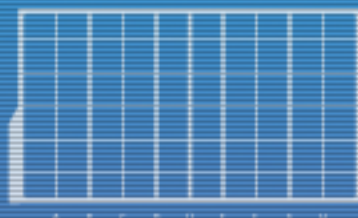
00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



DISCS

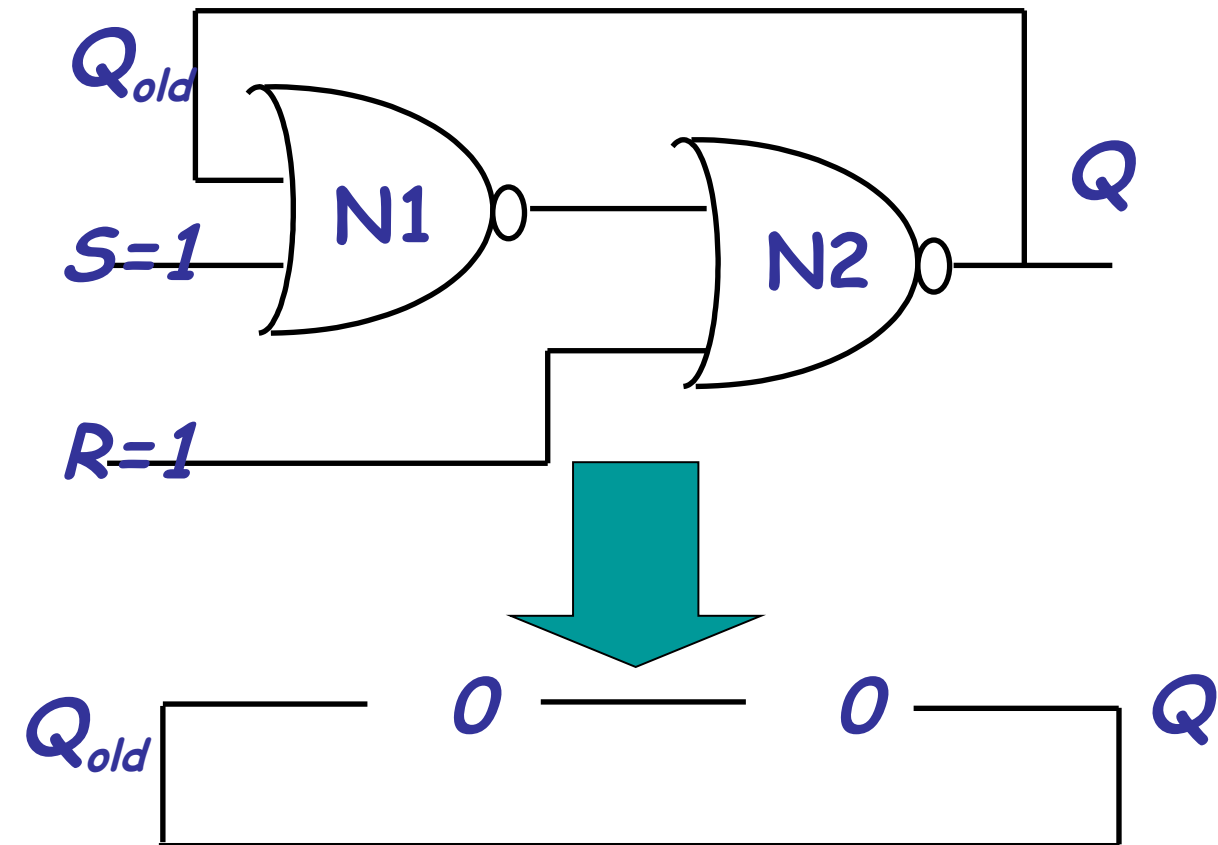
# NOR-NOR SR Latch

- ▶ **S=1, R=1 (avoid)**
  - ▶ results in  $Q = 0$ , BUT, cannot *safely* switch back to  $S=0, R=0$




$S$	$R$	$Q$
$0$	$0$	$Q_{old}$
$0$	$1$	$0$
$1$	$0$	$1$
$1$	$1$	$0$

 00101010010101000011110100001100  
10001100100001111001101010010101  
110010101010100001001100101010100  
1001010010010010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
100101010101010101010101010101



 
# NOR-NOR SR Latch

- ▶ To use, either **SET** ( $S=1, R=0$ ), or **RESET** ( $S=0, R=1$ ).
- ▶ Then, hold.
  - ▶ Long enough for signals to propagate around loop.
- ▶ Then, **LATCH** by setting  $S=0, R=0$ .
- ▶ **NEVER** go from  $S=1, R=1$  to  $S=0, R=0$ !
  - ▶ Both  $S$  and  $R$  are changing.
  - ▶ No way to know which one will get latched.
  - ▶ Possible metastable state if caught at forbidden values!



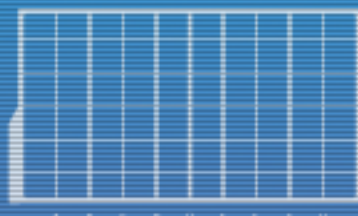
00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS



# S-R Latch Timing

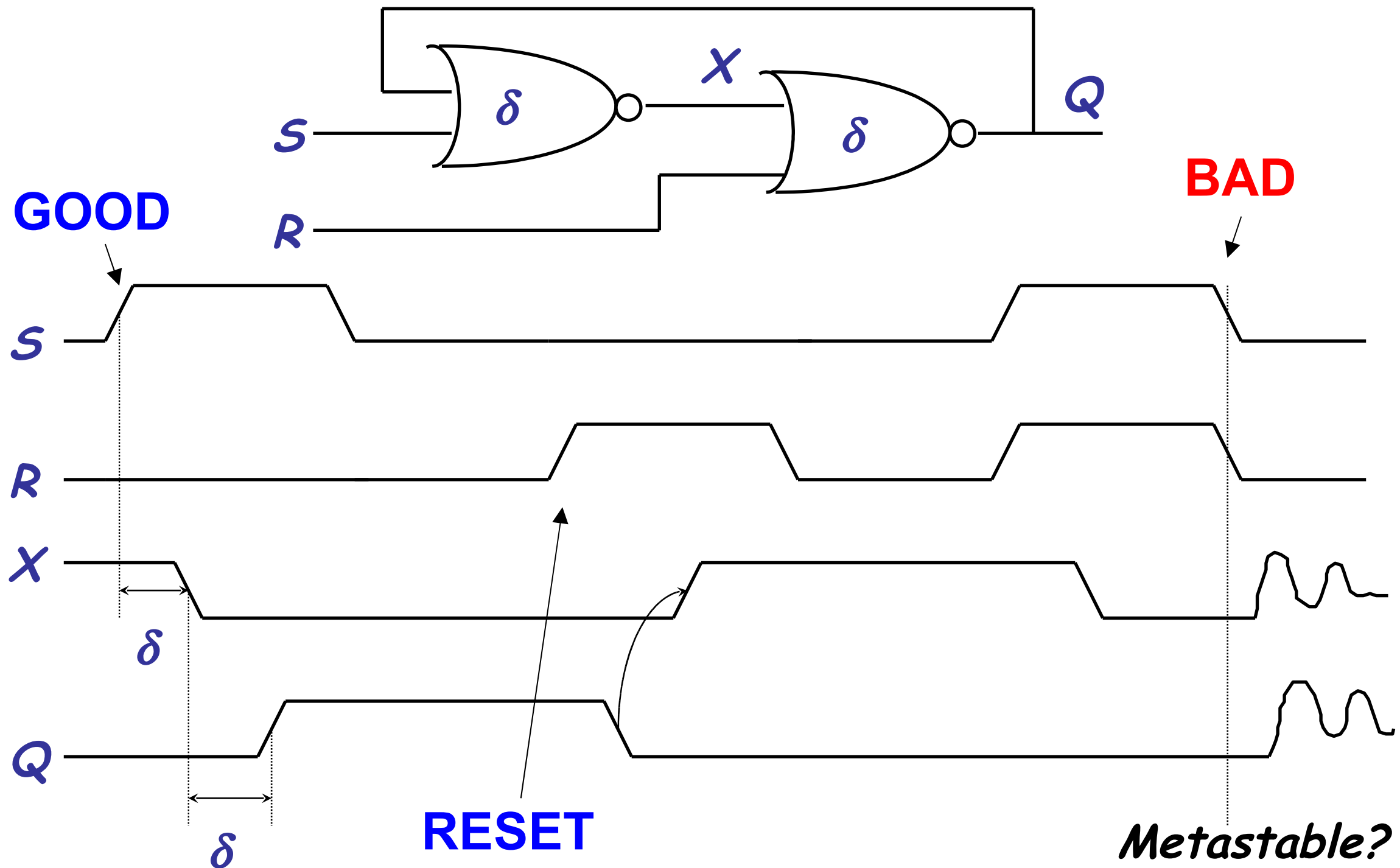

 00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS
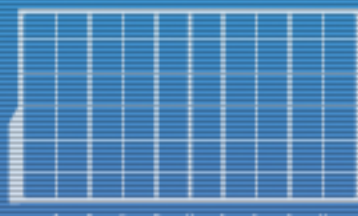
# Timing Rules


- ▶ As much as possible, only one input can change “at the same time”.
  - ▶ Single input change or SIC rule.
- ▶ We also should allow input transitions only after state has settled!
  - ▶ We risk corrupting output if input changes while state/output is not yet stable.
  - ▶ This constraint will be quantified in terms of setup time and hold time.

00101010010101000011110100001100  
10001100100001111001101010010101  
110010101010101000010011001010100  
1001010010010010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




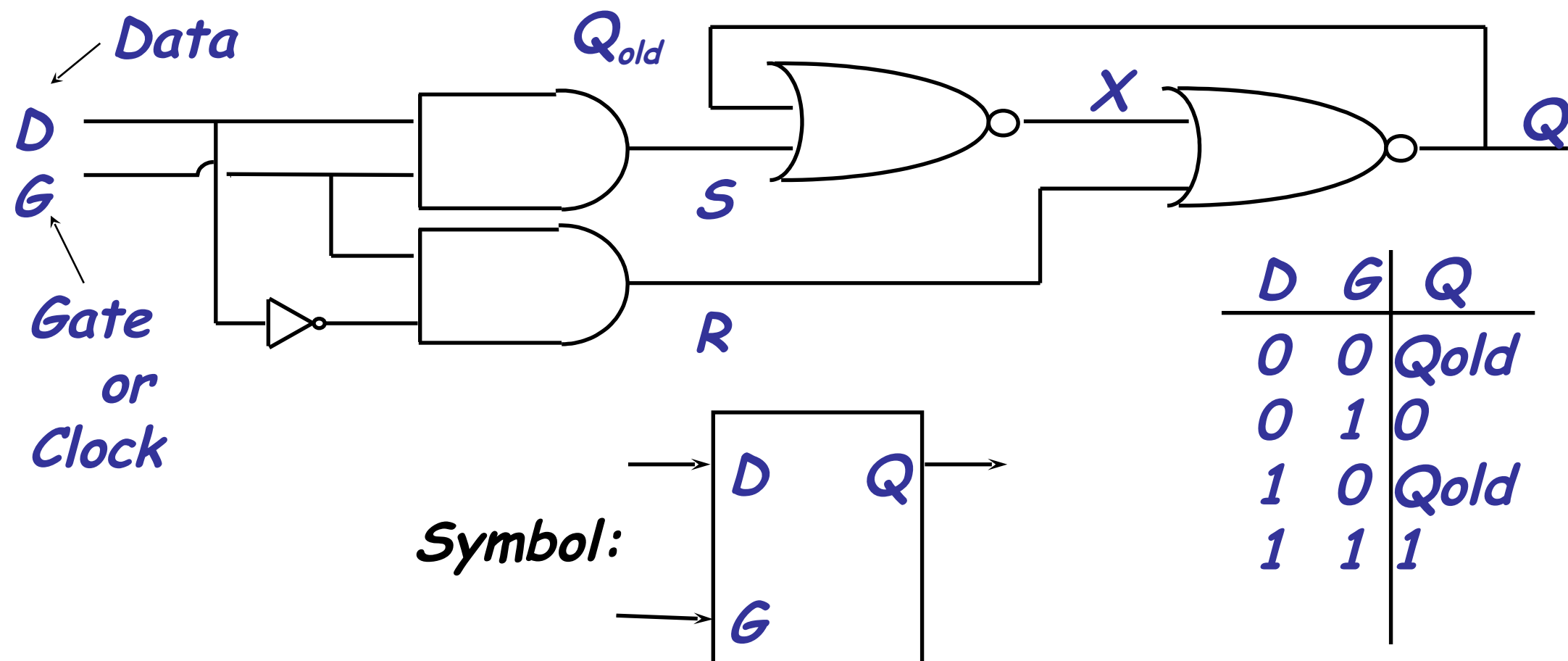
# D-Latch or Transparent Latch

- ▶ If Gate is 0, then both S and R = 0.
- ▶ If Gate is 1, then  $S = D$ ,  $R = \sim D$ .
  - ▶ Also,  $Q = D$ , hence the name.



  
# Another implementation of D-Latch

- ▶ Can be seen as a mux loop:
  - ▶  $Q = D$ , if  $G=1$  “transparent”.
  - ▶  $Q = Q_{old}$  if  $G=0$  “latched”.
- ▶ Or, can be seen as a “gate”:
  - ▶  $G=1$  “open”
  - ▶  $G=0$  “closed”
- ▶ Different from CMOS transmission gate because it has memory.
  - ▶ Transmission gate outputs hi-Z (disconnected) when closed .
  - ▶ D-latch outputs old value.



 
00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



DISCS




# Timing of D-Latch

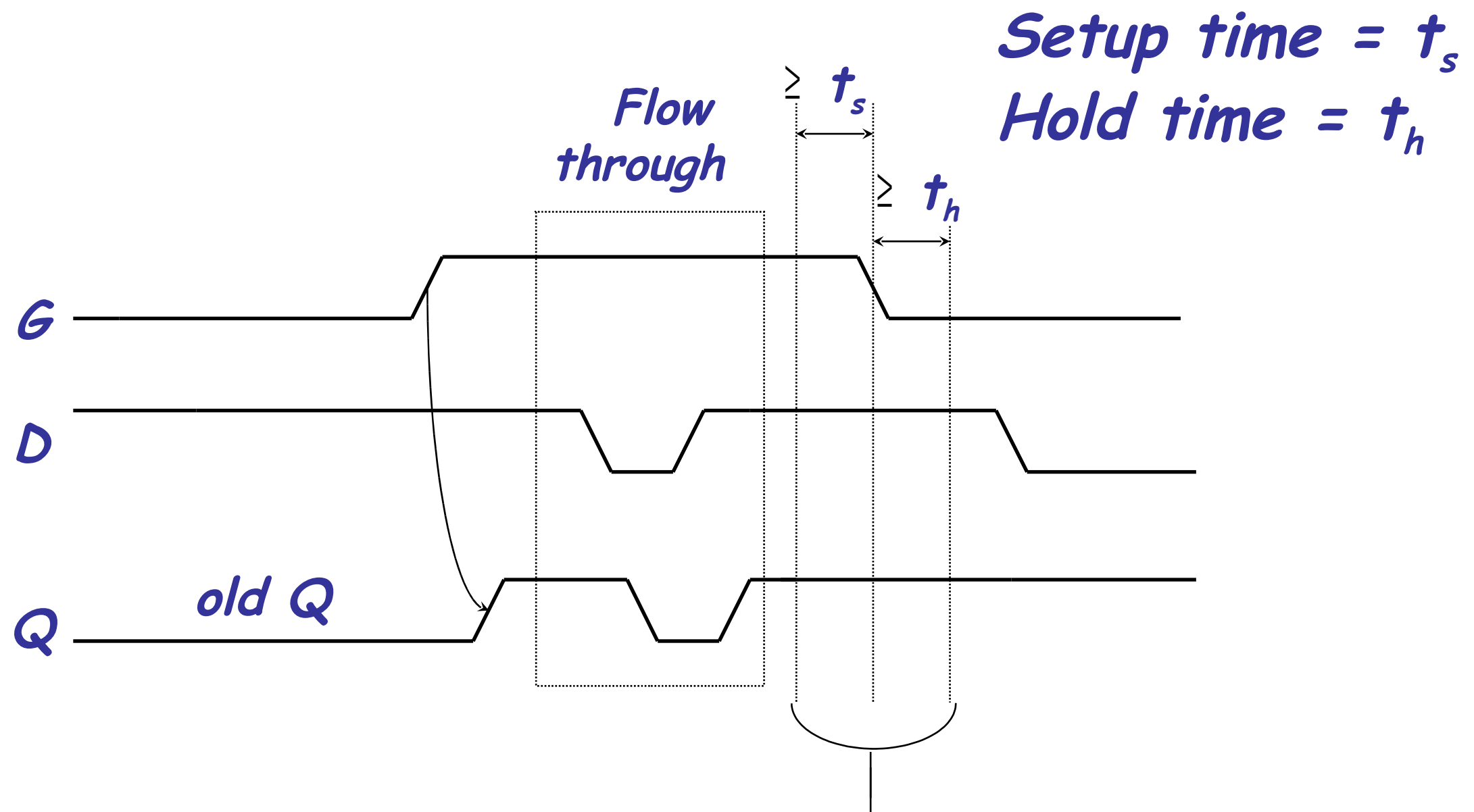

*D must not change in this region*

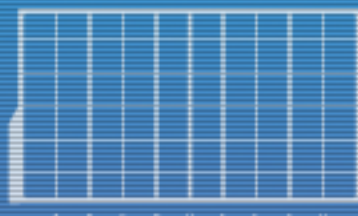
00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS
 
# Reality Bites: Hazards

- In combinational logic, we don't care what happens between  $t_{cd}$  and  $t_{pd}$ .




 00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010100101010010100101010010101



 
# Reality Bites: Hazards

- But what happens when we add a feedback loop? (e.g., mux loop D-latch)



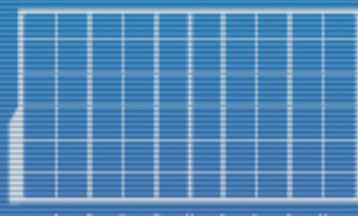
00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010100101010010100101010010101



DISCS
 
# Fixing Hazards

- ▶ Hazard due to input moving from DG to GQ.
  - ▶ Inputs to OR *momentarily* both 0, due to delays.
    - ▶ “Glitch” in OR output.
- ▶ Think of patches as “umbrellas”.
  - ▶ We “get wet” crossing from patch to patch.
- ▶ Solution: Add patches to cover gaps!



*Karnaugh Map:*


		$\bar{G}Q$			
		00	01	11	10
$D$	0	0	1	0	0
	1	0	1	1	1

$DG$


 
# Fixing Hazards

- ▶ Add patches to cover gaps in K-map.
  - ▶ Now, OR gate output is held high by DQ when crossing from DG to GQ.
- ▶ Assumes *hazard-free (glitch-free) gates*.
  - ▶ No glitches due to irrelevant inputs.
  - ▶ No glitches due to SIC.
    - ▶ e.g., OR output stable at 1, as long as at least 1 input is 1 – regardless of how the other 2 inputs change.




		$\bar{G}Q$				
		$GQ$	00	01	11	10
$D$	0		0	1	0	0
	1		0	1	1	1
		$DQ$				

Labels: DG (top right), DQ (bottom center)

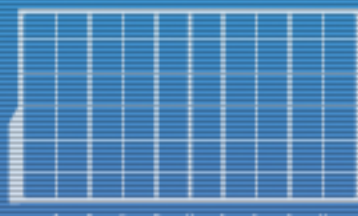
# Hazards Synopsis

- ▶ **Hazards:** “Glitches” in output behavior *even if we follow SIC rule.*
  - ▶ If SIC is not followed, then glitches are hard to avoid because of race conditions (think of the inputs as starting positions).
  - ▶ Hazards are glitches that occur *even if only one input is changed.*
- ▶ **Problem:** If glitches are part of feedback loop, then bad values propagate!
  - ▶ Results include oscillations, metastability, wrong values, etc.
- ▶ **Solution:** Cover gaps in K-map.
  - ▶ Add gates to connect all patches .
  - ▶ Protects against SIC hazards only.

```
00101010010101000011110100001100
10001100100001111001101010010101
110010101010101000010011001010100
1001010010010010101010101010101
11100001111010110000000111101001
001001010100101001001010010010110
10010100100001010100100101001010
10010100101010010100101010010101
10010101010101010101010101010101
```




# Reality Bites (Again)

 


- In reality, setup and hold times are not only dependent on contamination and propagation delays of gates, but also of wires.
- Exhaustive transistor-level simulation is required to determine setup and hold times accurately – But we won't worry about that.

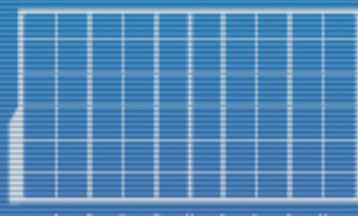
0010101001010100011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



# Edge-Triggered Flip-Flop

 


*Symbol:*

 

*aka register or  
"Positive-edge-  
triggered FF"*

$D$	$CLK$	$Q$
$\{0, 1\}$	0	$Q_{old}$
$\{0, 1\}$	1	$Q_{old}$
$D$	$\uparrow$	$D$
$\{0, 1\}$	$\downarrow$	$Q_{old}$

 0010101001010100011110100001100  
10001100100001111001101010010101  
110010101010100001001100101010100  
1001010010010010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010100101010010100101010010101




DISCS




# Edge-Triggered Flip-Flop

*D must not change in this region*

 


*Setup time =  $t_s$*   
*Hold time =  $t_h$*

 00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101




DISCS

# Latches and Flip-Flops

 


 *D-Latch: like a toll-gate, transparent when  $G=1$ .*





*FF: like an air-lock, never transparent except at clock edge.*

 
00101010010101000011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



# S-R Latch


 
 


 00101010010101000011110100001100  
 10001100100001111001101010010101  
 110010101010100001001100101010100  
 1001010010010010101010101010101  
 11100001111010110000000111101001  
 001001010100101001001010010010110  
 10010100100001010100100101001010  
 10010100101010010100101010010101  
 100101010101001010101010010101




DISCS

# D-Latch

   



# Edge-Triggered Flip-Flop

 


Setup time =  $t_s$

Hold time =  $t_h$


Clk-Q prop. =  $t_{pdC-Q}$

Clk-Q cont. =  $t_{cdC-Q}$

 Assume that setup and hold times are satisfied!



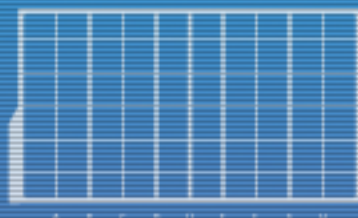0010101001010100011110100001100  
10001100100001111001101010010101  
11001010101010100001001100101010100  
100101001001001010101010101010101  
11100001111010110000000111101001  
001001010100101001001010010010110  
10010100100001010100100101001010  
10010100101010010100101010010101  
10010101010101010101010101010101



DISCS